

Lab #2: VHDL Components

Lab 2 is due Monday, April 3. Your lab report and source code must be submitted by **10:10 AM** before class. The late policy applies to this lab project. This lab is to be done in **teams**. Each team member should be involved in each problem, e.g., one developing implementation models while the other building test benchmarks. Get started early! The required format for lab reports can be found on the resource page.

Problem 1

Develop a behavioral VHDL model for a 4-to-1 word multiplexer (MUX). Your model should work with arbitrary length words; i.e., you should not place hard constraints on the lengths of inputs and outputs. Develop a test bench for your MUX that demonstrates each function **for all possible permutations of inputs other than the 4 words**.

Problem 2

Develop a behavioral VHDL model for a x -bit, 1-to- 2^y de-multiplexer, x and y being two parameters. Your device should include an ENABLE signal as well as normal inputs and outputs. Develop a test bench for your VHDL de-multiplexer model that demonstrates basic functionality. Simulate your design with one specific set of (x,y) and demonstrate correctness **for all possible permutations of inputs other than the words**.

Problem 3

(a) Develop a behavioral VHDL model for a 4-bit shift register. Your shift register should implement functions for LOAD, HOLD, RIGHT SHIFT and LEFT SHIFT. In addition to regular inputs, your shift register should provide a SHIFT LEFT INPUT and a SHIFT RIGHT INPUT that input the value shifted into the right-most and left-most bits, respectively. Your register should also include an ENABLE input and a CLOCK input. **The LOAD, HOLD, RIGHT SHIFT and the LEFT SHIFT functions should be rising-edge triggered.** Develop a test bench for your VHDL shift register that demonstrates each function for all possible combinations of input signals of "I_SHIFT_IN", "sel", "clock", "enable", and at least two values of "I". *shift_reg.vhdl* is a sample shift_reg program that only declares the interface. A sample test bench that tests only two input cases is provided in the file *shift_reg_tb.vhdl*.

(b) Use your 4-bit shift register from (a) to implement a structural VHDL model for an 8-bit shift register. This device should perform the same functions as the 4-bit shift register, but over 8 bits. Develop a test bench for your shift register that demonstrates each function for all possible combinations of input signals of "I_SHIFT_IN", "shift", "clock", "enable", "load", and two values of "I".

Problem 4

Design and implement a 4-bit integer adder/subtractor. The inputs are signed, that means the most significant bit represents the sign of number, 0 for positive and 1 for negative. The negative inputs are represented with two's complement format. The inputs of the components are two 4-bit signal vectors, and its outputs include a 4-bit signed signal vector for result, 1 bit carry (overflow) signal and 1 bit underflow signal. You may use any sequential or parallel digital algorithms for the add/subtract operations. Note that you can NOT use the "+" and "-" operators in your implementation.

Use synthesizable features of VHDL

You should try to use only the synthesizable features of VHDL. In particular, only one "wait" statement is allowed in a process. The "wait for" statements are not allowed in your implementation, but might be used in your test benches.

How to test using a VHDL simulator

You can use any VHDL simulator for this project. Choices include FreeHDL, GHDL and Xilinx Vivado simulator. Below is an example process with FreeHDL.

FreeHDL

GVHDL is the command of the package freehdl. Freehdl can be downloaded from <http://www.freehdl.seul.org> and install on Linux, Windows and MacOS. If it is an Ubuntu system, you can install it with the command “sudo apt-get install freehdl”. If you use a Windows 10 machine, you can install “windows subsystem for linux”, which is basically an Ubuntu Linux system.

Assuming we have "shift_reg.vhdl", which is the implementation of a 4-bit shift register, and "shift_reg_tb.vhdl", which is the test bench for our implementation, there are three steps to run the test bench:

1. Generate the executable for the test bench:
“gyhdl shift_reg.vhdl shift_reg_tb.vhdl --libieee”
2. Run the test bench:
"shift_reg_tb"
The most used commands are:
c <number> : execute cycles = execute <number> simulation cycles
n : next = execute next simulation cycle
q : quit = quit simulation
r <time> : run = execute simulation for <time>
d : dump = dump signals

GHDL

If you want to use GHDL, you can download it from <http://ghdl.free.fr>. The site provides pre-compiled packages for Linux, Windows and MacOS. You can also download the source and compile/install from there.

How to use GHDL

Assume GHDL is installed under the directory /usr/local/bin. Assuming we have "shift_reg.vhdl", which is the implementation of a 4-bit shift register, and "shift_reg_tb.vhdl", which is the test bench for our implementation, there are three steps to run the test bench:

- (1) Analyze: Compile the two vhd files
"/usr/local/bin/ghdl -a shift_reg.vhdl"
"/usr/local/bin/ghdl -a shift_reg_tb.vhdl"

If you use any IEEE libraries, add "--ieee= standard" after "-a".

- (2) Generate the executable for the test bench:
"/usr/local/bin/ghdl -e shift_reg_tb"

If you use any IEEE libraries, add "--ieee= standard" after "-e".

- (3) Run the test bench:
"/usr/local/bin/ghdl -r shift_reg_tb"

If you want to dump waveform files, add “--vcd=shift_reg.vcd”. You can use “gtkwave” or any other waveform viewers to open the “shift_reg.vcd” file.

What to Turn In

For this lab project, turn in all of your source code, including the code that implements the components, and the code that tests your implementations. Describe your testing methodology, and where applicable, explain why you select the input values that are used to test your implementation.

Peer evaluation: Please email your peer evaluation (guideline is on the resource page) of your teammates, including scores and justification, directly to the TA.